

## CAPACITANCE AND DIELECTRICS

24.1. IDENTIFY:  $C = \frac{Q}{V_{ab}}$

SET UP:  $1 \mu\text{F} = 10^{-6} \text{ F}$

EXECUTE:  $Q = CV_{ab} = (7.28 \times 10^{-6} \text{ F})(25.0 \text{ V}) = 1.82 \times 10^{-4} \text{ C} = 182 \mu\text{C}$

EVALUATE: One plate has charge  $+Q$  and the other has charge  $-Q$ .

24.5. IDENTIFY:  $C = \frac{Q}{V_{ab}}$ .  $C = \frac{\epsilon_0 A}{d}$ .

SET UP: When the capacitor is connected to the battery,  $V_{ab} = 12.0 \text{ V}$ .

EXECUTE: (a)  $Q = CV_{ab} = (10.0 \times 10^{-6} \text{ F})(12.0 \text{ V}) = 1.20 \times 10^{-4} \text{ C} = 120 \mu\text{C}$

(b) When  $d$  is doubled  $C$  is halved, so  $Q$  is halved.  $Q = 60 \mu\text{C}$ .

(c) If  $r$  is doubled,  $A$  increases by a factor of 4.  $C$  increases by a factor of 4 and  $Q$  increases by a factor of 4.  $Q = 480 \mu\text{C}$ .

EVALUATE: When the plates are moved apart, less charge on the plates is required to produce the same potential difference. With the separation of the plates constant, the electric field must remain constant to produce the same potential difference. The electric field depends on the surface charge density,  $\sigma$ . To produce the same  $\sigma$ , more charge is required when the area increases.

24.14. IDENTIFY: The capacitors between  $b$  and  $c$  are in parallel. This combination is in series with the 15 pF capacitor.

SET UP: Let  $C_1 = 15 \text{ pF}$ ,  $C_2 = 9.0 \text{ pF}$  and  $C_3 = 11 \text{ pF}$ .

EXECUTE: (a) For capacitors in parallel,  $C_{\text{eq}} = C_1 + C_2 + \dots$  so  $C_{23} = C_2 + C_3 = 20 \text{ pF}$


(b)  $C_1 = 15 \text{ pF}$  is in series with  $C_{23} = 20 \text{ pF}$ . For capacitors in series,  $\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$  so  $\frac{1}{C_{123}} = \frac{1}{C_1} + \frac{1}{C_{23}}$  and

$$C_{123} = \frac{C_1 C_{23}}{C_1 + C_{23}} = \frac{(15 \text{ pF})(20 \text{ pF})}{15 \text{ pF} + 20 \text{ pF}} = 8.6 \text{ pF}.$$

EVALUATE: For capacitors in parallel the equivalent capacitance is larger than any of the individual capacitors. For capacitors in series the equivalent capacitance is smaller than any of the individual capacitors.

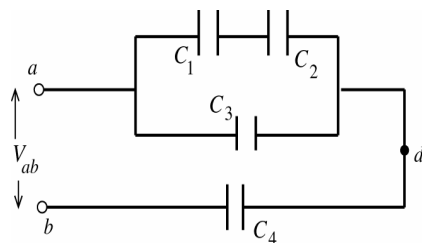24.15. IDENTIFY: Replace series and parallel combinations of capacitors by their equivalents. In each equivalent network apply the rules for  $Q$  and  $V$  for capacitors in series and parallel; start with the simplest network and work back to the original circuit.

SET UP: Do parts (a) and (b) together. The capacitor network is drawn in Figure 24.15a.



$$C_1 = C_2 = C_3 = C_4 = 400 \mu\text{F}$$

$$V_{ab} = 28.0 \text{ V}$$

Figure 24.15a

EXECUTE: Simplify the circuit by replacing the capacitor combinations by their equivalents:  $C_1$  and  $C_2$  are in series and are equivalent to  $C_{12}$  (Figure 24.15b).

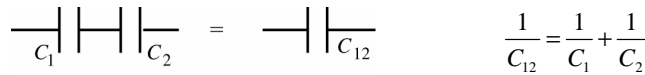


Figure 24.15b

$$C_{12} = \frac{C_1 C_2}{C_1 + C_2} = \frac{(4.00 \times 10^{-6} \text{ F})(4.00 \times 10^{-6} \text{ F})}{4.00 \times 10^{-6} \text{ F} + 4.00 \times 10^{-6} \text{ F}} = 2.00 \times 10^{-6} \text{ F}$$

$C_{12}$  and  $C_3$  are in parallel and are equivalent to  $C_{123}$  (Figure 24.15c).

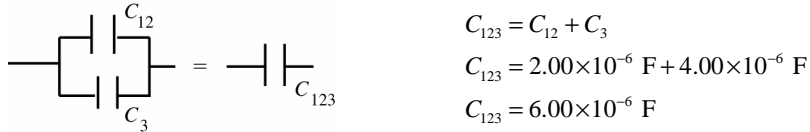


Figure 24.15c

$C_{123}$  and  $C_4$  are in series and are equivalent to  $C_{1234}$  (Figure 24.15d).

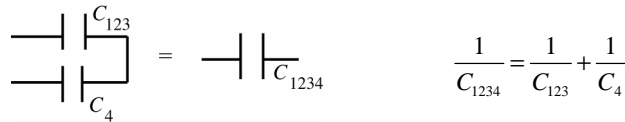


Figure 24.15d

$$C_{1234} = \frac{C_{123} C_4}{C_{123} + C_4} = \frac{(6.00 \times 10^{-6} \text{ F})(4.00 \times 10^{-6} \text{ F})}{6.00 \times 10^{-6} \text{ F} + 4.00 \times 10^{-6} \text{ F}} = 2.40 \times 10^{-6} \text{ F}$$

The circuit is equivalent to the circuit shown in Figure 24.15e.

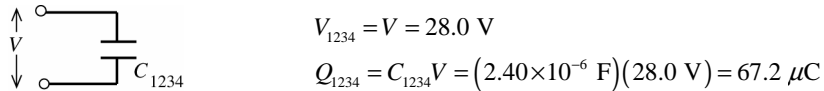


Figure 24.15e

Now build back up the original circuit, step by step.  $C_{1234}$  represents  $C_{123}$  and  $C_4$  in series (Figure 24.15f).

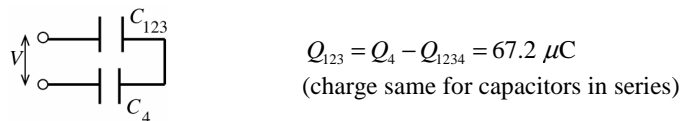


Figure 24.15f

$$\text{Then } V_{123} = \frac{Q_{123}}{C_{123}} = \frac{67.2 \mu\text{C}}{6.00 \mu\text{F}} = 11.2 \text{ V}$$

$$V_4 = \frac{Q_4}{C_4} = \frac{67.2 \mu\text{C}}{4.00 \mu\text{F}} = 16.8 \text{ V}$$

Note that  $V_4 + V_{123} = 16.8 \text{ V} + 11.2 \text{ V} = 28.0 \text{ V}$ , as it should.

Next consider the circuit as written in Figure 24.15g.

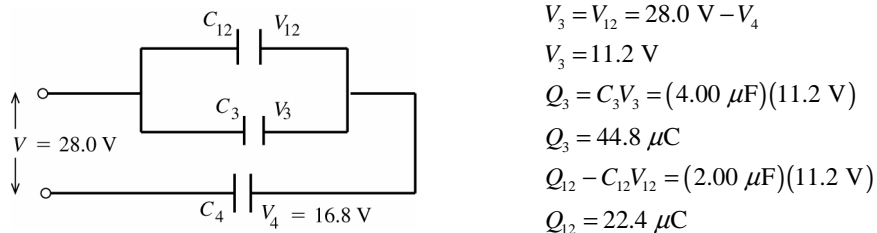
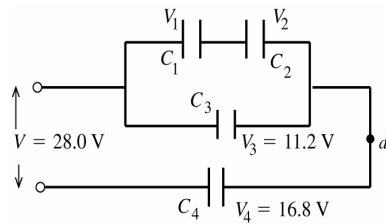


Figure 24.15g

Finally, consider the original circuit, as shown in Figure 24.15h.


**Figure 24.15h**

Note that  $V_1 + V_2 = 11.2 \text{ V}$ , which equals  $V_3$  as it should.

Summary:  $Q_1 = 22.4 \mu\text{C}$ ,  $V_1 = 5.6 \text{ V}$

$Q_2 = 22.4 \mu\text{C}$ ,  $V_2 = 5.6 \text{ V}$

$Q_3 = 44.8 \mu\text{C}$ ,  $V_3 = 11.2 \text{ V}$

$Q_4 = 67.2 \mu\text{C}$ ,  $V_4 = 16.8 \text{ V}$

(c)  $V_{ad} = V_3 = 11.2 \text{ V}$

**EVALUATE:**  $V_1 + V_2 + V_4 = V$ , or  $V_3 + V_4 = V$ .  $Q_1 = Q_2$ ,  $Q_1 + Q_3 = Q_4$  and  $Q_4 = Q_{1234}$ .

$Q_1 = Q_2 = Q_{12} = 22.4 \mu\text{C}$   
(charge same for capacitors in series)

$$V_1 = \frac{Q_1}{C_1} = \frac{22.4 \mu\text{C}}{4.00 \mu\text{F}} = 5.6 \text{ V}$$

$$V_2 = \frac{Q_2}{C_2} = \frac{22.4 \mu\text{C}}{4.00 \mu\text{F}} = 5.6 \text{ V}$$

**24.18. IDENTIFY:** For capacitors in parallel the voltages are the same and the charges add. For capacitors in series, the charges are the same and the voltages add.  $C = Q/V$ .

**SET UP:**  $C_1$  and  $C_2$  are in parallel and  $C_3$  is in series with the parallel combination of  $C_1$  and  $C_2$ .

**EXECUTE:** (a)  $C_1$  and  $C_2$  are in parallel and so have the same potential across them:

$$V_1 = V_2 = \frac{Q_2}{C_2} = \frac{40.0 \times 10^{-6} \text{ C}}{3.00 \times 10^{-6} \text{ F}} = 13.33 \text{ V}. \text{ Therefore, } Q_1 = V_1 C_1 = (13.33 \text{ V})(3.00 \times 10^{-6} \text{ F}) = 80.0 \times 10^{-6} \text{ C}. \text{ Since } C_3 \text{ is}$$

in series with the parallel combination of  $C_1$  and  $C_2$ , its charge must be equal to their combined charge:

$$C_3 = 40.0 \times 10^{-6} \text{ C} + 80.0 \times 10^{-6} \text{ C} = 120.0 \times 10^{-6} \text{ C}.$$

(b) The total capacitance is found from  $\frac{1}{C_{\text{tot}}} = \frac{1}{C_{12}} + \frac{1}{C_3} = \frac{1}{9.00 \times 10^{-6} \text{ F}} + \frac{1}{5.00 \times 10^{-6} \text{ F}}$  and  $C_{\text{tot}} = 3.21 \mu\text{F}$ .

$$V_{ab} = \frac{Q_{\text{tot}}}{C_{\text{tot}}} = \frac{120.0 \times 10^{-6} \text{ C}}{3.21 \times 10^{-6} \text{ F}} = 37.4 \text{ V}.$$

**EVALUATE:**  $V_3 = \frac{Q_3}{C_3} = \frac{120.0 \times 10^{-6} \text{ C}}{5.00 \times 10^{-6} \text{ F}} = 24.0 \text{ V}$ .  $V_{ab} = V_1 + V_3$ .

**24.22. IDENTIFY:** Simplify the network by replacing series and parallel combinations of capacitors by their equivalents.

**SET UP:** For capacitors in series the voltages add and the charges are the same;  $\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$  For capacitors

in parallel the voltages are the same and the charges add;  $C_{\text{eq}} = C_1 + C_2 + \dots$   $C = \frac{Q}{V}$ .

**EXECUTE:** (a) The equivalent capacitance of the  $5.0 \mu\text{F}$  and  $8.0 \mu\text{F}$  capacitors in parallel is  $13.0 \mu\text{F}$ . When these two capacitors are replaced by their equivalent we get the network sketched in Figure 24.22. The equivalent capacitance of these three capacitors in series is  $3.47 \mu\text{F}$ .


(b)  $Q_{\text{tot}} = C_{\text{tot}} V = (3.47 \mu\text{F})(50.0 \text{ V}) = 174 \mu\text{C}$

(c)  $Q_{\text{tot}}$  is the same as  $Q$  for each of the capacitors in the series combination shown in Figure 24.22, so  $Q$  for each of the capacitors is  $174 \mu\text{C}$ .

**EVALUATE:** The voltages across each capacitor in Figure 24.22 are  $V_{10} = \frac{Q_{\text{tot}}}{C_{10}} = 17.4 \text{ V}$ ,  $V_{13} = \frac{Q_{\text{tot}}}{C_{13}} = 13.4 \text{ V}$  and

$V_9 = \frac{Q_{\text{tot}}}{C_9} = 19.3 \text{ V}$ .  $V_{10} + V_{13} + V_9 = 17.4 \text{ V} + 13.4 \text{ V} + 19.3 \text{ V} = 50.1 \text{ V}$ . The sum of the voltages equals the applied

voltage, apart from a small difference due to rounding.

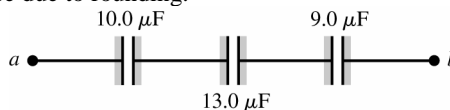
**Figure 24.22**

**24.32. IDENTIFY:** The two capacitors are in series.  $\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$ .  $C = \frac{Q}{V}$ .  $U = \frac{1}{2}CV^2$ .

**SET UP:** For capacitors in series the voltages add and the charges are the same.

**EXECUTE:** (a)  $\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2}$  so  $C_{\text{eq}} = \frac{C_1 C_2}{C_1 + C_2} = \frac{(150 \text{ nF})(120 \text{ nF})}{150 \text{ nF} + 120 \text{ nF}} = 66.7 \text{ nF}$ .

$$Q = CV = (66.7 \text{ nF})(36 \text{ V}) = 2.4 \times 10^{-6} \text{ C} = 2.4 \mu\text{C}$$

(b)  $Q = 2.4 \mu\text{C}$  for each capacitor.

$$(c) U = \frac{1}{2}C_{\text{eq}}V^2 = \frac{1}{2}(66.7 \times 10^{-9} \text{ F})(36 \text{ V})^2 = 43.2 \mu\text{J}$$

(d) We know  $C$  and  $Q$  for each capacitor so rewrite  $U$  in terms of these quantities.  $U = \frac{1}{2}CV^2 = \frac{1}{2}C(Q/C)^2 = Q^2/2C$

$$150 \text{ nF: } U = \frac{(2.4 \times 10^{-6} \text{ C})^2}{2(150 \times 10^{-9} \text{ F})} = 19.2 \mu\text{J}; 120 \text{ nF: } U = \frac{(2.4 \times 10^{-6} \text{ C})^2}{2(120 \times 10^{-9} \text{ F})} = 24.0 \mu\text{J}$$

Note that  $19.2 \mu\text{J} + 24.0 \mu\text{J} = 43.2 \mu\text{J}$ , the total stored energy calculated in part (c).

$$(e) 150 \text{ nF: } V = \frac{Q}{C} = \frac{2.4 \times 10^{-6} \text{ C}}{150 \times 10^{-9} \text{ F}} = 16 \text{ V}; 120 \text{ nF: } V = \frac{Q}{C} = \frac{2.4 \times 10^{-6} \text{ C}}{120 \times 10^{-9} \text{ F}} = 20 \text{ V}$$

Note that these two voltages sum to 36 V, the voltage applied across the network.

**EVALUATE:** Since  $Q$  is the same the capacitor with smaller  $C$  stores more energy ( $U = Q^2/2C$ ) and has a larger voltage ( $V = Q/C$ ).

**24.57. IDENTIFY:** Simplify the network by replacing series and parallel combinations by their equivalent. The stored energy in a capacitor is  $U = \frac{1}{2}CV^2$ .

**SET UP:** For capacitors in series the voltages add and the charges are the same;  $\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$ . For capacitors

in parallel the voltages are the same and the charges add;  $C_{\text{eq}} = C_1 + C_2 + \dots$ .  $C = \frac{Q}{V}$ .  $U = \frac{1}{2}CV^2$ .

**EXECUTE:** (a) Find  $C_{\text{eq}}$  for the network by replacing each series or parallel combination by its equivalent. The successive simplified circuits are shown in Figure 24.57a–c.

$$U_{\text{tot}} = \frac{1}{2}C_{\text{eq}}V^2 = \frac{1}{2}(2.19 \times 10^{-6} \text{ F})(12.0 \text{ V})^2 = 1.58 \times 10^{-4} \text{ J} = 158 \mu\text{J}$$

(b) From Figure 24.57c,  $Q_{\text{tot}} = C_{\text{eq}}V = (2.19 \times 10^{-6} \text{ F})(12.0 \text{ V}) = 2.63 \times 10^{-5} \text{ C}$ . From Figure 24.57b,  $Q_{\text{tot}} = 2.63 \times 10^{-5} \text{ C}$ .

$$V_{4.8} = \frac{Q_{4.8}}{C_{4.8}} = \frac{2.63 \times 10^{-5} \text{ C}}{4.80 \times 10^{-6} \text{ F}} = 5.48 \text{ V}. U_{4.8} = \frac{1}{2}CV^2 = \frac{1}{2}(4.80 \times 10^{-6} \text{ F})(5.48 \text{ V})^2 = 7.21 \times 10^{-5} \text{ J} = 72.1 \mu\text{J}$$

This one capacitor stores nearly half the total stored energy.

**EVALUATE:**  $U = \frac{Q^2}{2C}$ . For capacitors in series the capacitor with the smallest  $C$  stores the greatest amount of energy.

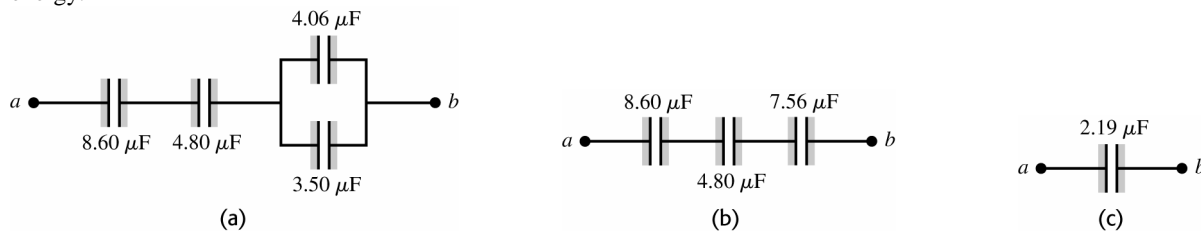


Figure 24.57

**24.58. IDENTIFY:** Apply the rules for combining capacitors in series and parallel. For capacitors in series the voltages add

**24.59. (a) IDENTIFY:** Replace series and parallel combinations of capacitors by their equivalents.

**SET UP:** The network is sketched in Figure 24.59a.

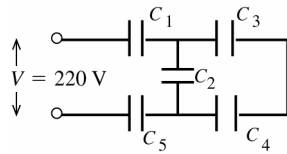


Figure 24.59a

$$C_1 = C_5 = 8.4 \mu\text{F}$$

$$C_2 = C_3 = C_4 = 4.2 \mu\text{F}$$

**EXECUTE:** Simplify the circuit by replacing the capacitor combinations by their equivalents:  $C_3$  and  $C_4$  are in series and can be replaced by  $C_{34}$  (Figure 24.59b):

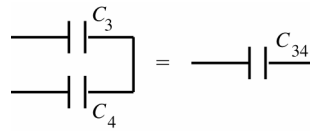


Figure 24.59b

$$\frac{1}{C_{34}} = \frac{1}{C_3} + \frac{1}{C_4}$$

$$\frac{1}{C_{34}} = \frac{C_3 + C_4}{C_3 C_4}$$

$$C_{34} = \frac{C_3 C_4}{C_3 + C_4} = \frac{(4.2 \mu\text{F})(4.2 \mu\text{F})}{4.2 \mu\text{F} + 4.2 \mu\text{F}} = 2.1 \mu\text{F}$$

$C_2$  and  $C_{34}$  are in parallel and can be replaced by their equivalent (Figure 24.59c):

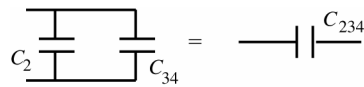


Figure 24.59c

$$C_{234} = C_2 + C_{34}$$

$$C_{234} = 4.2 \mu\text{F} + 2.1 \mu\text{F}$$

$$C_{234} = 6.3 \mu\text{F}$$

$C_1$ ,  $C_5$  and  $C_{234}$  are in series and can be replaced by  $C_{\text{eq}}$  (Figure 24.59d):

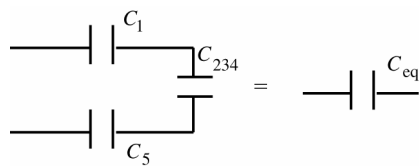


Figure 24.59d

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_5} + \frac{1}{C_{234}}$$


$$\frac{1}{C_{\text{eq}}} = \frac{2}{8.4 \mu\text{F}} + \frac{1}{6.3 \mu\text{F}}$$

$$C_{\text{eq}} = 2.5 \mu\text{F}$$

**EVALUATE:** For capacitors in series the equivalent capacitor is smaller than any of those in series. For capacitors in parallel the equivalent capacitance is larger than any of those in parallel.

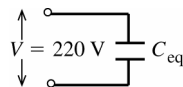**(b) IDENTIFY and SET UP:** In each equivalent network apply the rules for  $Q$  and  $V$  for capacitors in series and parallel; start with the simplest network and work back to the original circuit.

**EXECUTE:** The equivalent circuit is drawn in Figure 24.59e.



$$Q_{\text{eq}} = C_{\text{eq}} V$$

$$Q_{\text{eq}} = (2.5 \mu\text{F})(220 \text{ V}) = 550 \mu\text{C}$$

Figure 24.59e

$$Q_1 = Q_5 = Q_{234} = 550 \mu\text{C} \text{ (capacitors in series have same charge)}$$

$$V_1 = \frac{Q_1}{C_1} = \frac{550 \mu\text{C}}{8.4 \mu\text{F}} = 65 \text{ V}$$

$$V_5 = \frac{Q_5}{C_5} = \frac{550 \mu\text{C}}{8.4 \mu\text{F}} = 65 \text{ V}$$

$$V_{234} = \frac{Q_{234}}{C_{234}} = \frac{550 \mu\text{C}}{6.3 \mu\text{F}} = 87 \text{ V}$$

Now draw the network as in Figure 24.59f.

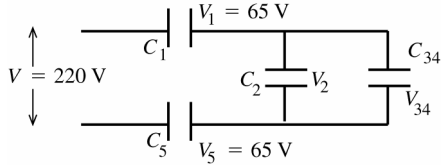


Figure 24.59f

$V_2 = V_{34} = V_{234} = 87 \text{ V}$   
 capacitors in parallel have the same potential

$$Q_2 = C_2 V_2 = (4.2 \mu\text{F})(87 \text{ V}) = 370 \mu\text{C}$$

$$Q_{34} = C_{34} V_{34} = (2.1 \mu\text{F})(87 \text{ V}) = 180 \mu\text{C}$$

Finally, consider the original circuit (Figure 24.59g).

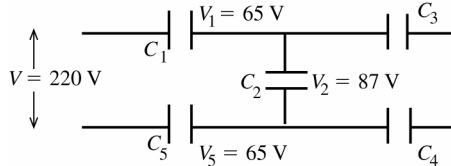


Figure 24.59g

$Q_3 = Q_4 = Q_{34} = 180 \mu\text{C}$   
 capacitors in series have the same charge

$$V_3 = \frac{Q_3}{C_3} = \frac{180 \mu\text{C}}{4.2 \mu\text{F}} = 43 \text{ V}$$

$$V_4 = \frac{Q_4}{C_4} = \frac{180 \mu\text{C}}{4.2 \mu\text{F}} = 43 \text{ V}$$

Summary:  $Q_1 = 550 \mu\text{C}$ ,  $V_1 = 65 \text{ V}$

$$Q_2 = 370 \mu\text{C}, V_2 = 87 \text{ V}$$

$$Q_3 = 180 \mu\text{C}, V_3 = 43 \text{ V}$$

$$Q_4 = 180 \mu\text{C}, V_4 = 43 \text{ V}$$

$$Q_5 = 550 \mu\text{C}, V_5 = 65 \text{ V}$$

**EVALUATE:**  $V_3 + V_4 = V_2$  and  $V_1 + V_2 + V_5 = 220 \text{ V}$  (apart from some small rounding error)

$$Q_1 = Q_2 + Q_3 \text{ and } Q_5 = Q_2 + Q_4$$